

Memory

RAM – Random Access Memory

- Used for storing variables for programs

ROM - Read Only Memory

- Typically used for booting

ROM and RAM both allow for random access

- RAM \Leftrightarrow read/write RAM
- ROM \Leftrightarrow read only RAM


How many gigs of RAM can a 32 bit OS use?

- 4 GB = 2^{32} = 4294967296 bytes



RAM Configuration

 - An $n \times m$ RAM has n locations each of size m
 - Example 4K x 128 :
 - 4096 locations (1K = 1024)
 - The data in each location is 128 bits long
 - m is the size of the d_in bus and the d_out bus
 - n and m have no relationship
 - The size of the address bus is $\log_2 n$. Each location has a unique address



VHDL for Simple RAM

```
entity raminfer is
    generic (addr_width  : integer := 6;    --default to a 64 x 256 RAM
            data_width   : integer := 8);
    port(
        clk    : in std_logic;
        we     : in std_logic;
        addr   : in std_logic_vector((addr_width - 1) downto 0);
        d_in   : in std_logic_vector(data_width - 1 downto 0);
        d_out  : out std_logic_vector(data_width - 1 downto 0));
end raminfer;

architecture rtl of raminfer is


    type ram_type is array ((2**addr_width - 1) downto 0) of std_logic_vector (data_width - 1 downto 0);
    signal RAM : ram_type;

begin
    process(clk)
    begin
        if (clk'event and clk = '1') then
            if (we = '1') then
                RAM(to_integer(unsigned(addr))) <= d_in;
            end if;
            d_out <= RAM(to_integer(unsigned(addr)));
        end if;
    end process;
end rtl;
```



RAM Synthesis

Flow Summary	
Flow Status	Successful - Sun Oct 26 14:20:11 2014
Quartus II 32-bit Version	13.0.1 Build 232 06/12/2013 SP 1 SJ Full Version
Revision Name	raminfer
Top-level Entity Name	raminfer
Family	Cyclone II
Device	EP2C35F672C6
Timing Models	Final
Total logic elements	0 / 33,216 (0 %)
Total combinational functions	0 / 33,216 (0 %)
Dedicated logic registers	0 / 33,216 (0 %)
Total registers	0
Total pins	82 / 475 (17 %)
Total virtual pins	0
Total memory bits	512 / 483,840 (< 1 %)
Embedded Multiplier 9-bit elements	0 / 70 (0 %)
Total PLLs	0 / 4 (0 %)


$$64 \times 8 = 512$$


Distributed RAM

- FPGA logic blocks have configurable lookup tables
- Each LUT can be used as a couple bits of RAM
- Many LUTs can be chained together to create a larger RAM block

Block RAM

- Dedicated memory containing several kilobytes of RAM

RAM RTL View

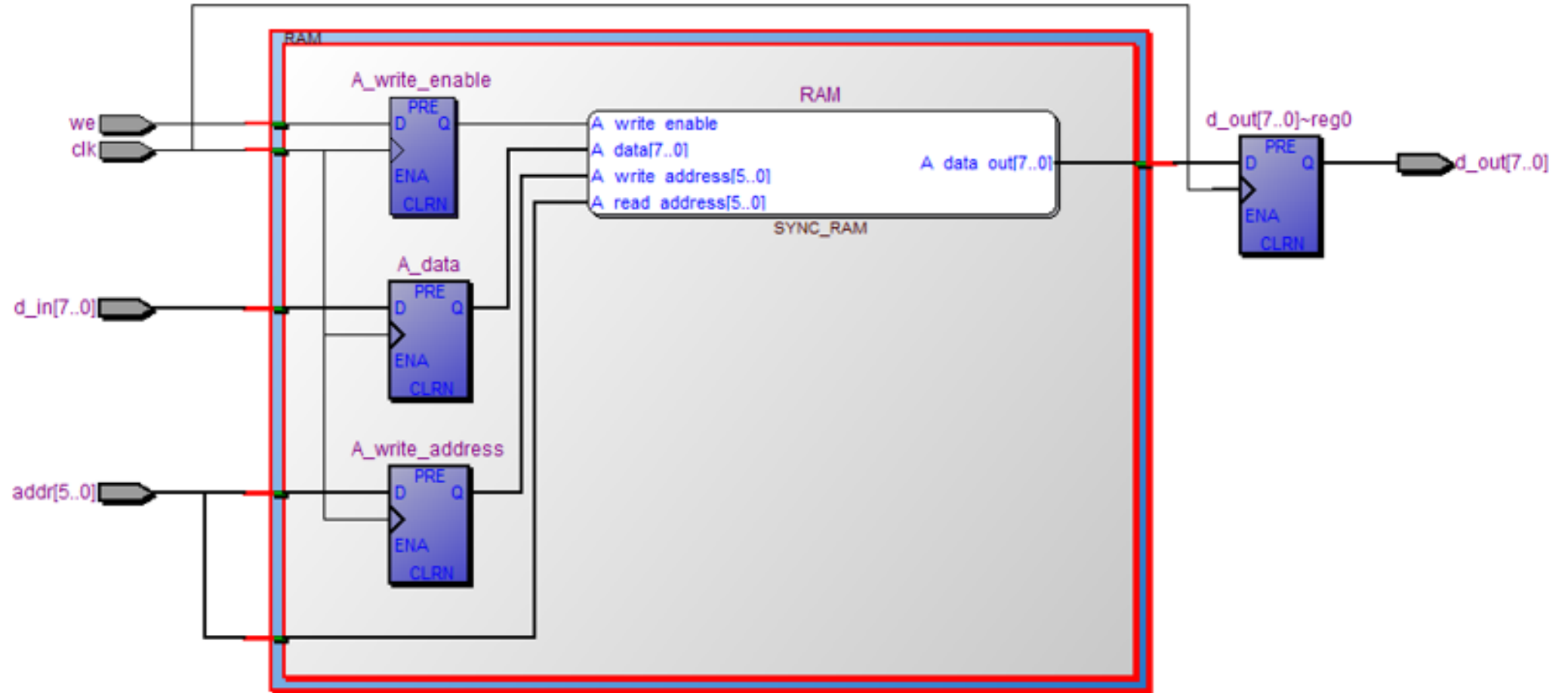

ROM

```
-- ENTITY DECLARATION
--
ENTITY hex_to_ssd IS
PORT(inputs      : IN  STD_LOGIC_VECTOR(3 DOWNTO 0);
      clk        : IN  STD_LOGIC;
      outputs     : OUT STD_LOGIC_VECTOR(6 DOWNTO 0));
END hex_to_ssd;
--
-- STRUCTURE ARCHITECTURE BODY
--
ARCHITECTURE structure OF hex_to_ssd IS

    TYPE SSD_array IS ARRAY(0 to 9) OF STD_LOGIC_VECTOR(6 DOWNTO 0);

    SIGNAL SSD: SSD_array := ("1000000", "1111001", "0100100", "0110000",
                             "0011001", "0010010", "0000010", "1111000",
                             "0000000", "0010000");

begin
process (clk)
begin
    if (rising_edge(clk)) then
        outputs <= SSD (to_integer(unsigned(inputs)));
    end if;
end process;
END structure;
```

How does ROM differ from RAM?

The configuration is the same ($n \times m$)

ROM is inferred when VHDL is written as a
look up table

case
array



ROM RTL View

